

Kingdom of Saudi Arabia المملكة العربية السعودية

Imam Muhammed Ibn Saud University جامعة الامام محمد بن سعود

College of Engineering كلية الهندسة

Electrical Engineering Dept قسم الهندسة الكهربائية

Electronic Devices & Applications Lab مختبر النبايطالالكترونيةوتطبيقاتها



Experiment No.9:RC Phase Shift Oscillator

Electronic Devices & Applications Lab EE324

Name : Abdulaziz Ali Abdul Munim

ID no. : 434006384

Date : 11/12/2017

Grade: _____

Experiment No.9: RC Phase Shift Oscillator

Objective:

To produce frequency without using input voltage and to Study the Oscillator.

Components:

- 1- OPAMP $\mu A741$
- 2- Bread Board.
- 3- DC Dual power supply.
- 4- Oscilloscope.
- 5- Capacitors & Resistors.

Theory:

The basic RC Oscillator which is also known as a Phase-shift Oscillator, produces a sine wave output signal using regenerative feedback obtained from the resistor-capacitor combination. This regenerative feedback from the RC network is due to the ability of the capacitor to store an electric charge.

This resistor-capacitor feedback network can be connected to produce a leading phase shift (phase advance network) or interchanged to produce a lagging phase shift (phase retard network) the outcome is still the same as the sine wave oscillations only occur at the frequency at which the overall phase-shift is 360° .

By varying one or more of the resistors or capacitors in the phase-shift network, the frequency can be varied and generally this is done by keeping the resistors the same and using a 3-ganged variable capacitor.

In a Resistance-Capacitance Oscillator or simply an RC Oscillator, we make use of the fact that a phase shift occurs between the input to a RC network and the output from the same network by using RC elements in the feedback branch, for example.

RC Phase-Shift Network: The circuit on the left shows a single resistor-capacitor network whose output voltage "leads" the input voltage by some angle less than 90° . An ideal single-pole RC circuit would produce a phase shift of exactly 90° , and because 180° of phase shift is required for oscillation, at least two

single-poles must be used in an *RC oscillator* design.

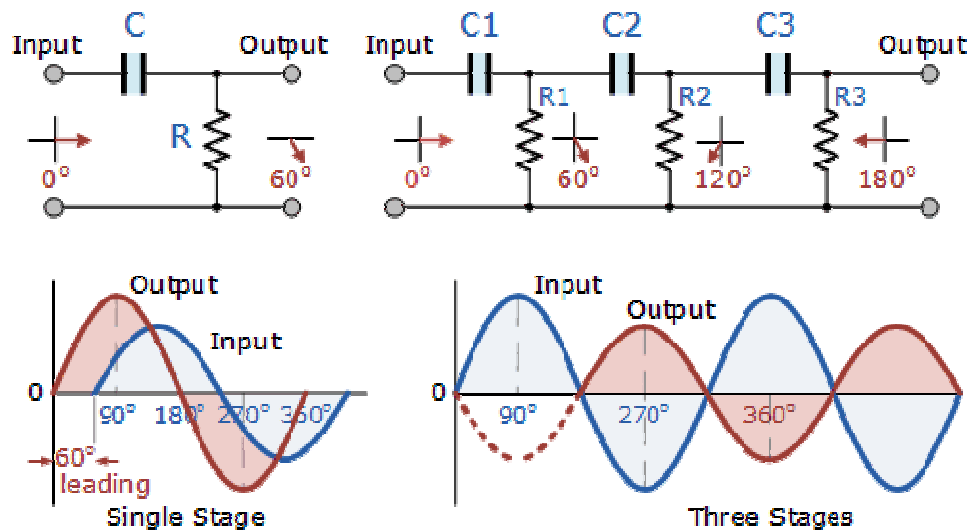


Fig.1: Phase Shift Network

Circuit Diagram:

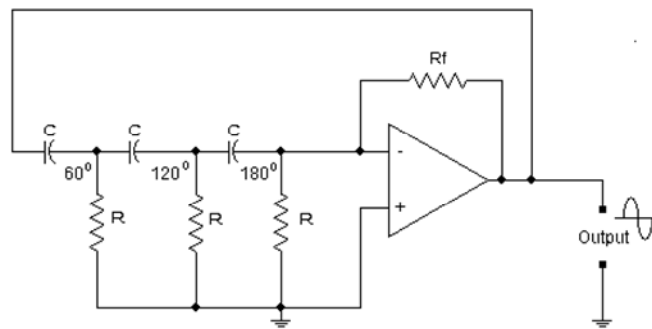


Figure 2: RC phase shift Oscillator using Op-amp

Procedure:

1. Construct the RC phase circuit on the breadboard as shown in the circuit diagram.
2. Use: $V_{++} = 14\text{ V}$, $V_{-} = -14\text{ V}$, $R_i = 10\text{ k}\Omega$, and $R_f = 470\text{ k}\Omega$.
3. Capacitor value is $0.0022\text{ }\mu\text{F}$.
4. Find f_c practically and theoretically.

Theoretical Frequency Calculation:

$$f_c = \frac{1}{2\pi RC\sqrt{6}} = \frac{1}{2\pi (10 K)(0.0022 \mu F)\sqrt{6}} = 2.95 \text{ kHz}$$

Observations:

Graph:

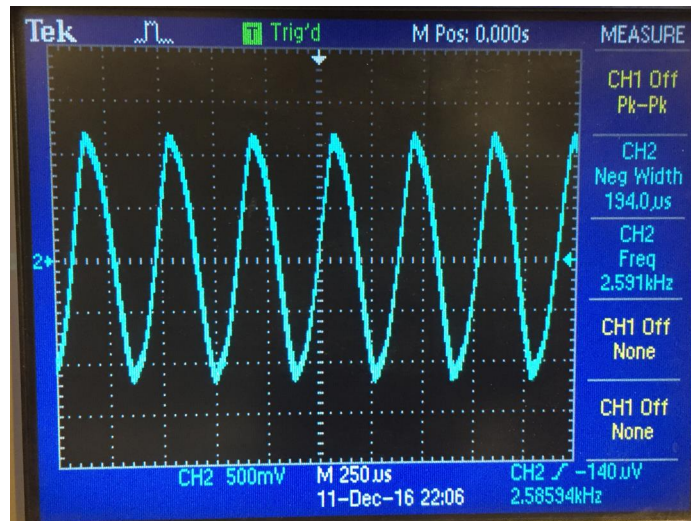


Fig.3: Output Wave with a Frequency =2.589KHz

Table1.1: Theoretical and Practical Frequencies of RCphase shift Oscillator

| Observations | |
|---|-----------|
| Theoretical Frequency of the Oscillator | =2.95KHz |
| Practical Frequency of the Oscillator | =2.589KHz |

Practical Frequency generated by RC Phase Shift Oscillator is $f_c=2.589\text{KHz}$

Conclusion:

The practical circuit of RC phase shift oscillator is successfully conducted, it has generated a sine wave of frequency $f_c=2.589\text{KHz}$, with an amplitude of $500\text{mV} \times 4.75 = 2.375 \text{ Volts}$

The error percentage is 11 %.