



Quiz Score:

15

Model Answer ..... اسم الطالب

**Problem I**

Two single phase loads connected in series have the following

$P_1 = 300W$        $Q_1 = 400 \text{ VAR (inductive)}$

$P_2 = 200W$        $Q_2 = 300 \text{ (capacitive)}$


Find the total PF

$I^2 R_1 = P_1$

$I^2 R_2 = P_2$

$\frac{R_1}{R_2} = \frac{3}{2}$

$\frac{x_1}{x_2} = \frac{4}{3}$

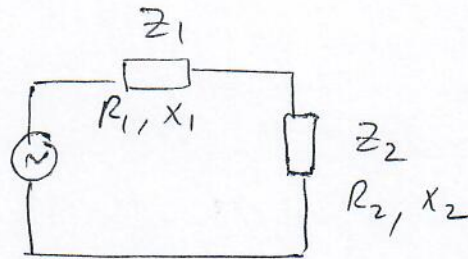


$P_t = P_1 + P_2 = 500W$

$I^2 x_1 = Q_1$

$I^2 x_2 = Q_2$

$Q_t = Q_1 - Q_2 = 100 \text{ VAR}$


2

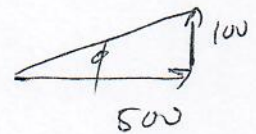

$PF = \cos \left( \sin^{-1} \frac{1}{5} \right) = 0.98$

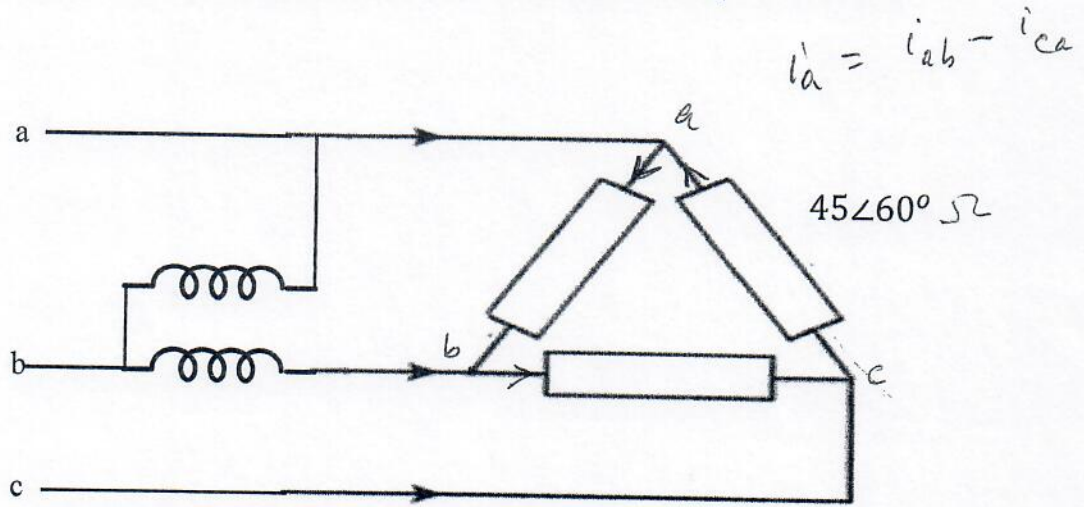**Problem II**


A wattmeter is connected to a balanced delta load as shown. If the source is 400 V with abc phase sequence, find the reading of the power meter.



$$i_b = i_{bc} - i_{ab}$$

$$V_{ba} = 400 \angle 180^\circ$$
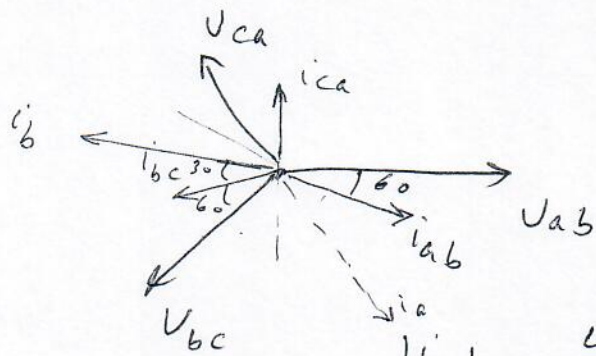
$$i_b = \frac{400}{45} \sqrt{3} \angle -120 - 90$$



$$|i_{ab}| = \frac{400}{45} \text{ A}$$

$$|i_b| = \frac{400}{45} \sqrt{3} \text{ A}$$

$$P = \frac{400}{45} \sqrt{3} * 400 \cos(180 + 120 + 90)$$

$390^\circ = 30^\circ$

$$= \frac{400}{45} * \frac{3}{2} * 400$$

$$= \del{3333} \text{ W} \quad 5333 \text{ W}$$

or Current ← power (2)  
(1)