



Quiz Score:

15

..... Model Answer اسم الطالب


A separately excited generator, when running at 1000 rpm supplied 200A at 125V (terminal voltage). What will be the load current when the speed drops to 800 rpm if I_f (field current) is unchanged? Given that the armature resistance = 0.04Ω .

$$\frac{E_{a1}}{E_{a2}} = \frac{1000}{800} = \frac{5}{4} \quad (1)$$

$$E_{a1} = 200(0.625 + 0.04) = 133V \quad (1)$$

$$E_{a2} = 106.4V \quad (1)$$
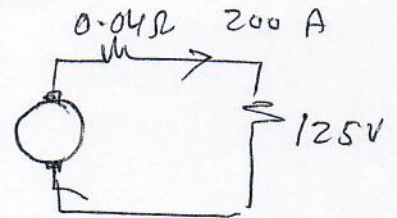
$$I_L = \frac{106.4}{0.665} = 160A \quad (1)$$



$$R_L = \frac{125}{200} = 0.625 \Omega \quad (1)$$