

## Quiz 2

An 8-pole D.C shunt generator with 778 wave-connected armature conductors and running at 500 r.p.m . supplies a load of  $12.5\Omega$  resistance at terminal voltage of 250 V. The armature resistance is  $0.24\Omega$  and the field resistance is  $250\Omega$ . Find the armature current, the induced e.m.f and the flux per pole.?

Solution:

Load current

$$I_L = \frac{V}{R} = \frac{250}{12.5} = 20 \text{ A}$$

Shunt current

$$I_f = \frac{250}{250} = 1 \text{ A}$$

Armature current

$$I_a = 20 + 1 = 21 \text{ A}$$

$$\text{Induce e.m.f} = 250 + (21 \times 0.24) = 255.04 \text{ V}$$

Now

$$E_g = \frac{Zn\phi}{60} \left( \frac{P}{a} \right)$$

$$a = 2 \quad (\text{wave-wound})$$

$$255.04 = \frac{778 \times 500 \times \phi}{60} \left( \frac{8}{2} \right)$$

$$\phi = 9.83 \text{ mWb.}$$